 


Half Adder

```
ado/Half Adder/Half Adder.srscs/sources_1/new/Design.v
// Code your design here
module ha(
  input a,b,
  output sum,carry
);
  assign sum = (a^b);
  assign carry = (a*b);
endmodule


D:/Vivado/Half Adder/Half Adder.srscs/sim_1/new/Testbench.v
// Code your testbench here
// or browse Examples
module ha_tb;
  reg a,b;
  wire sum,carry;
  ha u1(.a(a),.b(b),.sum(sum),.carry(carry));
  initial begin
    $monitor("a=%b,b=%b, ,sum=%b,carry=%b",a,b,sum,carry);
    a=1'b0;b=1'b0;#10;
    a=1'b0;b=1'b1;#10;
    a=1'b1;b=1'b0;#10;
    a=1'b1;b=1'b1;#10;
  end
endmodule
```

Timing Diagram



Digram

e

 

OUTPUT

```
# KERNEL: a=0,b=0, ,sum=0,carry=0
# KERNEL: a=0,b=1, ,sum=1,carry=0
# KERNEL: a=1,b=0, ,sum=1,carry=0
# KERNEL: a=1,b=1, ,sum=0,carry=1
```

A **Half Adder** is a basic combinational logic circuit designed to add two single-bit binary numbers. It produces two outputs: the **sum** and the **carry**.

Inputs and Outputs

- **Inputs:** Two single-bit binary digits, usually labeled A and B.
- **Outputs:**
 - **Sum (S):** The least significant bit of the addition result.

- **Carry (C):** The carry-out bit, which is generated when both inputs are 1.

How It Works

The half adder adds the two input bits according to binary addition rules:

- $0 + 0 = \text{Sum } 0, \text{ Carry } 0$
- $0 + 1 = \text{Sum } 1, \text{ Carry } 0$
- $1 + 0 = \text{Sum } 1, \text{ Carry } 0$
- $1 + 1 = \text{Sum } 0, \text{ Carry } 1$ (since $1 + 1 = 10$ in binary)

Logic Gates Used

- The **Sum (S)** output is obtained using an **XOR gate** because the sum is 1 only when the inputs differ.
- The **Carry (C)** output is obtained using an **AND gate** because carry is 1 only when both inputs are 1.

Truth Table

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0

A	B	Sum (S)	Carry (C)
1	1	0	1

Boolean Expressions

- Sum: $S = A \oplus B$
- Carry: $C = A \cdot B$

Circuit Diagram

The half adder circuit consists of one XOR gate for the sum and one AND gate for the carry, connected to the two inputs A and B.

Limitations

- The half adder cannot handle a carry input from a previous addition, so it cannot be used alone for multi-bit binary addition.
- For multi-bit addition, **full adders** (which include carry-in inputs) are used, often constructed by combining two half adders and an OR gate.

Applications

- Used as a fundamental building block in digital circuits.
- Forms the basis for constructing full adders.
- Used in arithmetic logic units (ALUs), binary counters, and other digital arithmetic circuits.

In summary, the half adder is a simple yet essential digital circuit that adds two single-bit binary numbers and provides the sum and carry outputs using XOR and AND gates respectively